


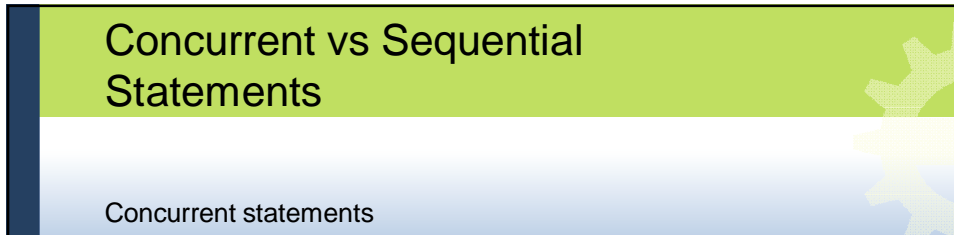
Lecture 7

VHDL (Part-2)

Concurrent and Sequential Statements, Loops



TAMPEREEN TEKNILLINEN YLIOPISTO




Concurrent vs Sequential Statements

Concurrent statements

- Simple signal assignment statement
- Conditional signal assignment statement
- Selected signal assignment statement

Sequential Statements


- VHDL process
- Sequential signal assignment statement
- Variable assignment statement
- If statement
- Case statement
- Simple for loop statement



TAMPEREEN TEKNILLINEN YLIOPISTO

2

Concurrent vs Sequential VHDL

 

Modeling Style	Concurrent	Sequential
Location	inside architecture	inside process
Example statements	process, component instance, concurrent signal assingment	if, for, switch-case, signal assignment

Section 1

CONCURRENT SIGNAL ASSIGNMENT STATEMENT

Architecture body

Simplified syntax

```
architecture arch_name of entity_name is
    declarations;
begin
    concurrent statement;
    concurrent statement;
    concurrent statement;
    . . .
end arch_name;
```

Simple Signal Assignment

Syntax:

```
signal_name <= projected_waveform;
```

- E.g.,


```
y <= a + b + 1 after 10 ns;
```

Examples

E.g.,

- status <= '1';
- even <= (p1 and p2) or (p3 and p4);
- arith_out <= a + b + c - 1;

Implementation of last statement

 

Conditional signal assignment statement

Syntax

```

signal_name <= value_expr_1 when boolean_expr_1 else
value_expr_2 when boolean_expr_2 else
value_expr_3 when boolean_expr_3 else
. . .
value_expr_n
  
```

E.g., 4-to-1 mux

input s	output x
00	a
01	b
10	c
11	d

```

library ieee;
use ieee.std_logic_1164.all;
entity mux4 is
  port(
    a,b,c,d: in std_logic_vector(7 downto 0);
    s: in std_logic_vector(1 downto 0);
    x: out std_logic_vector(7 downto 0)
  );
end mux4 ;
architecture cond_arch of mux4 is
begin
  x <= a when (s="00") else
    b when (s="01") else
    c when (s="10") else
    d;
end cond_arch;

```



TAMPEREEN TEKNILLINEN YLIOPISTO

9

E.g., 4-to-2 priority encoder

input r	output code	active
1---	11	1
01--	10	1
001-	01	1
0001	00	1
0000	00	0

```

entity prio_encoder42 is
  port(
    r: in std_logic_vector(3 downto 0);
    code: out std_logic_vector(1 downto 0);
    active: out std_logic
  );
end prio_encoder42;
architecture cond_arch of prio_encoder42 is
begin
  code <= "11" when (r(3)='1') else
    "10" when (r(2)='1') else
    "01" when (r(1)='1') else
    "00";
  active <= r(3) or r(2) or r(1) or r(0);
end cond_arch ;

```




TAMPEREEN TEKNILLINEN YLIOPISTO

10


Conceptual representation
 
```
signal_name <= value_expr_1 when boolean_expr_1 else
value_expr_2;
```



 Examples

```
signal_name <= value_expr_1 when boolean_expr_1 else
value_expr_2 when boolean_expr_2 else
value_expr_3 when boolean_expr_3 else
value_expr_4;
```




ALU

E.g.

```
signal a,b,r: unsigned(7 downto 0);
signal s: std_logic_vector(1 downto 0);
```

```
with s select
```

```
  r <= a+1  when "11",
      a-b-1  when "10",
      a+b    when others;
```

 

Section 2

SEQUENTIAL SIGNAL ASSIGNMENT STATEMENTS


Sequential vs. Concurrent

```

architecture x of entity is
  declaration
  begin
    concurrent statement;
    concurrent statement;
    process()
    begin
      sequential statement;
      sequential statement;
    end
    concurrent statement;
    process()
    begin
      sequential statement;
      sequential statement;
    end
  end
end x;
  
```

Diagram illustrating the distinction between concurrent and sequential statements in VHDL. Blue arrows point to concurrent statements (top two lines, the `begin` block of the first process, and the second process), while a red arrow points to a sequential statement (the first line inside the first process). Labels "concurrent" and "sequential!" are placed next to their respective arrows.

Conceptual implementation

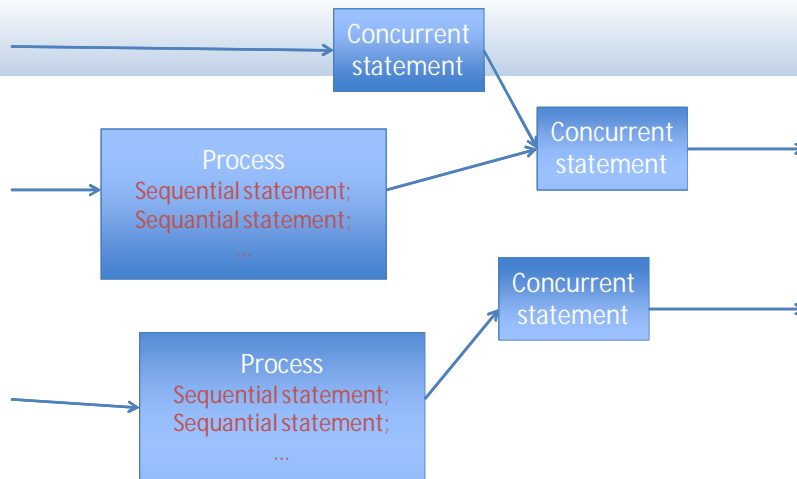


VHDL Process

Contains a set of sequential statements to be executed sequentially
 The whole process is a concurrent statement
 Can be interpreted as a circuit part enclosed inside of a black box

Two types of process

 - A process with a sensitivity list
- A process with wait statement



A process with a sensitivity list

Syntax

```
process(sensitivity_list)
  declarations;
begin
  sequential statement;
  sequential statement;
  . . .
end process;
```

A process is like a circuit part,
 which can be

- active (known as *activated*)
- inactive (known as *suspended*).

A process is activated when a
 signal in the sensitivity list
 changes its value

Its statements will be executed
 sequentially until the end of the
 process

Example

E.g, 3-input and circuit

```
signal a,b,c,y: std_logic;
process(a,b,c)
begin
    y <= a and b and c;
end process;
```

How to interpret this:

```
process(a)
begin
    y <= a and b and c;
end process;
```

For a combinational circuit, all input should be included in the sensitivity list



Sequential Signal Assignment Statement

Syntax

```
signal_name <= value_expression;
```

Syntax is identical to the simple concurrent signal assignment

Caution:

- Inside a process, a signal can be assigned multiple times, but only the last assignment takes effect



Examples

E.g.,

```
process(a,b,c,d)
Begin y <= a or c;
      y <= a and b;
      y <= c and d;
end process;
```

It is same as

```
process(a,b,c,d)
begin
  y <= c and d;
end process;
```

IF statement

Syntax

```
if boolean_expr_1 then
  sequential_statements;
elsif boolean_expr_2 then
  sequential_statements;
elsif boolean_expr_3 then
  sequential_statements;
  . . .
else
  sequential_statements;
end if;
```

E.g., 4-to-1 mux

input	output
s	x
00	a
01	b
10	c
11	d

```

architecture if_arch of mux4 is
begin
  process (a,b,c,d,s)
  begin
    if (s="00") then
      x <= a;
    elsif (s="01") then
      x <= b;
    elsif (s="10") then
      x <= c;
    else
      x <= d;
    end if;
  end process;
end if_arch;

```

Comparison to conditional signal assignment

Two statements are the same if there is only one output signal in if statement

If statement is more flexible

Sequential statements can be used in then, elsif and else branches:

- Multiple statements
- Nested if statements

```

sig <= value_expr_1 when boolean_expr_1 else
value_expr_2 when boolean_expr_2 else
value_expr_3 when boolean_expr_3 else
. . .
value_expr_n;

```

It can be written as

```

process (...)
  if boolean_expr_1 then
    sig <= value_expr_1;
  elsif boolean_expr_2 then
    sig <= value_expr_2;
  elsif boolean_expr_3 then
    sig <= value_expr_3;
  . . .
  else
    sig <= value_expr_n;
  end if;
end process

```

Incomplete branch and incomplete signal assignment

According to VHDL definition:

- Only the “then” branch is required; “elsif” and “else” branches are optional
- When a signal is unassigned due to omission, it keeps the “previous value” (implying “memory”)

Incomplete branch

E.g.,

```
process (a, b)
begin
  if (a=b) then
    eq <= '1';
  end if ;
end process;
```

It implies

```
process (a, b)
begin
  if (a=b) then
    eq <= '1';
  else
    eq <= eq;
  end if ;
end process
```

Incomplete branch (cont'd)

Fix

```
process (a,b)
begin
  if (a=b) then
    eq <= '1';
  else
    eq <= '0';
  end if ;
end process
```

Incomplete signal assignment

E.g.,

```
process (a,b)
begin
  if (a>b) then
    gt <= '1';
  elsif (a=b) then
    eq <= '1';
  else
    lt <= '1';
  end if ;
end process ;
```

Fixes

```

process (a,b)
begin
  if (a>b) then
    gt <= '1';
    eq <= '0';
    lt <= '0';
  elsif (a=b) then
    gt <= '0';
    eq <= '1';
    lt <= '0';
  else
    gt <= '0';
    eq <= '0';
    lt <= '1';
  end if;
end process;

```

```

process (a,b)
begin
  gt <= '0';
  eq <= '0';
  lt <= '0';
  if (a>b) then
    gt <= '1';
  elsif (a=b) then
    eq <= '1';
  else
    lt <= '1';
  end if;
end process;

```

Conceptual implementation

Same as conditional signal assignment statement if the if statement consists of


- One output signal
- One sequential signal assignment in each branch

Multiple sequential statements can be constructed recursively

```

if boolean_expr then
  sig_a <= value_expr_a_1;
  sig_b <= value_expr_b_1
else
  sig_a <= value_expr_a_2;
  sig_b <= value_expr_b_2;
end if;

```

 

Case statement

Syntax

```

case case_expression is
  when choice_1 =>
    sequential statements;
  when choice_2 =>
    sequential statements;
  . . .
  when choice_n =>
    sequential statements;
end case;

```

E.g., 4-to-1 mux

input	output
s	x
00	a
01	b
10	c
11	d

```

architecture case_arch of mux4 is
begin
  process (a,b,c,d,s)
  begin
    case s is
      when "00" =>
        x <= a;
      when "01" =>
        x <= b;
      when "10" =>
        x <= c;
      when others =>
        x <= d;
    end case;
  end process;
end case_arch;

```


Comparison to selected signal assignment

Two statements are the same if there is only one output signal in case statement

Case statement is more flexible

Sequential statements can be used in choice branches

```
with sel_exp select
  sig <= value_expr_1 when choice_1,
        value_expr_2 when choice_2,
        value_expr_3 when choice_3,
        . . .
        value_expr_n when choice_n;
```

It can be rewritten as:

```
case sel_exp is
  when choice_1 =>
    sig <= value_expr_1;
  when choice_2 =>
    sig <= value_expr_2;
  when choice_3 =>
    sig <= value_expr_3;
  . . .

  when choice_n =>
    sig <= value_expr_n;
end case;
```



Incomplete signal assignment

According to VHDL definition:

- When a signal is unassigned, it keeps the “previous value” (implying “memory”)

```
process (a)
  case a is
    when "100"|"101"|"110"|"111" =>
      high <= '1';
    when "010"|"011" =>
      middle <= '1';
    when others =>
      low <= '1';
  end case;
end process;
```



Fixes

```

process (a)
  case a is
    when "100"|"101"|"110"|"111" =>
      high <= '1';
      middle <= '0';
      low <= '0';
    when "010"|"011" =>
      high <= '0';
      middle <= '1';
      low <= '0';
    when others =>
      high <= '0';
      middle <= '0';
      low <= '1';
    end case;
  end process;

```

```

process (a)
  high <= '0';
  middle <= '0';
  low <= '0';
  case a is
    when "100"|"101"|"110"|"111" =>
      high <= '1';
    when "010"|"011" =>
      middle <= '1';
    when others =>
      low <= '1';
    end case;
  end process;

```



TAMPEREEN TEKNILLINEN YLIOPISTO

35

Conceptual implementation

Same as selected signal assignment statement if the case statement consists of


- One output signal
- One sequential signal assignment in each branch

Multiple sequential statements can be constructed recursively

```

case case_exp is
  when c0 =>
    sig_a <= value_expr_a_0;
    sig_b <= value_expr_b_0;
  when c1 =>
    sig_a <= value_expr_a_1;
    sig_b <= value_expr_b_1;
  when others =>
    sig_a <= value_expr_a_n;
    sig_b <= value_expr_b_n;
end case;

```

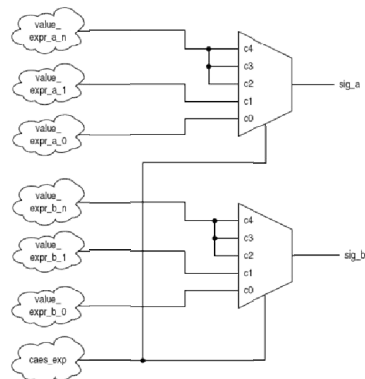

TAMPEREEN TEKNILLINEN YLIOPISTO

36

Simple for loop statement

VHDL provides a variety of loop constructs

Only a restricted form of loop can be synthesized

Syntax of simple for loop:

```
for index in loop_range loop  
    sequential statements;  
end loop;
```

loop_range must be static

Index assumes value of loop_range from left to right

Loops: example

Hardware:

```
add_i: for i in 0 to max_c-1 generate  
    b(i) <= a(i) + i;  
end generate add_i;
```

Generates <max_c> parallel computation units

E.g., bit-wide xor

```

library ieee;
use ieee.std_logic_1164.all;

entity wide_xor is
  port(
    a, b: in std_logic_vector(3 downto 0);
    y: out std_logic_vector(3 downto 0)
  );
end wide_xor;

architecture demo_arch of wide_xor is
  constant WIDTH: integer := 4;
begin
  process(a, b)
  begin
    for i in (WIDTH-1) downto 0 loop
      y(i) <= a(i) xor b(i);
    end loop;
  end process;
end demo_arch;

```

Conceptual implementation

“Unroll” the loop

For loop should be treated as “shorthand” for repetitive statements

E.g., bit-wise xor

```

y(3) <= a(3) xor b(3);
y(2) <= a(2) xor b(2);
y(1) <= a(1) xor b(1);
y(0) <= a(0) xor b(0);

```

E.g., reduced-xor

```

library ieee;
use ieee.std_logic_1164.all;

entity reduced_xor_demo is
  port(
    a: in std_logic_vector(3 downto 0);
    y: out std_logic
  );
end reduced_xor_demo;

architecture demo_arch of reduced_xor_demo is
  constant WIDTH: integer := 4;
  signal tmp: std_logic_vector(WIDTH-1 downto 0);
begin
  process(a, tmp)
  begin
    tmp(0) <= a(0);  -- boundary bit
    for i in 1 to (WIDTH-1) loop
      tmp(i) <= a(i) xor tmp(i-1);
    end loop;
  end process;
  y <= tmp(WIDTH-1);
end demo_arch;

```

Summary

Concurrent vs. sequential statement

Concurrent

- simple assignment
- selected assignment
- conditional assignment

Sequential

- Processes
- If statement
- Case statement
- Loop statement